
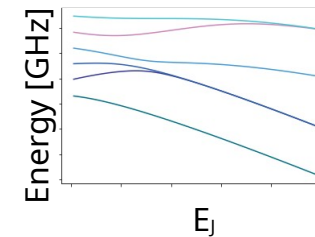



Circuit Quantization and Diagonalization

with scqubits

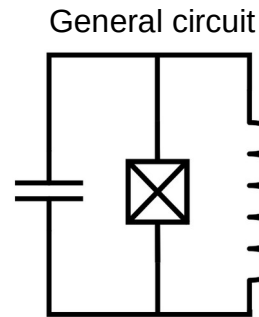

Sai Pavan Chitta
Northwestern University

Outline

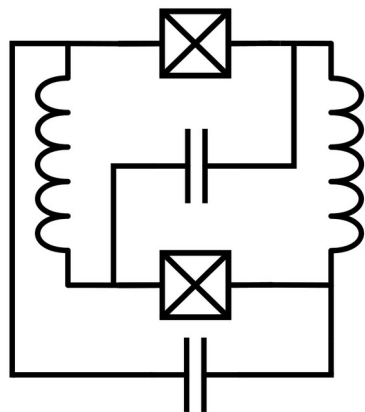

$$\mathcal{L}(\{\theta_i, \dot{\theta}_i\}; \Phi_{\text{ext}}, n_g)$$

Canonical quantization



$$H(\{Q_i, \theta_i\})$$

→ Challenges:

- Identification of the boundary conditions
- Appropriate variable choice

Boundary Conditions and Variable Classification



→ Boundary conditions:

- affect the nature of Hilbert space
- influence the choice of basis states


→ How do we get to the boundary conditions? - Potential

→ Degree of Freedom (DoF): periodic and extended


$$E_J \cos(\varphi)$$

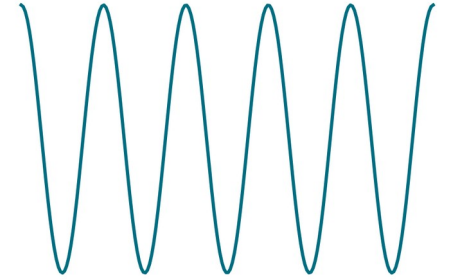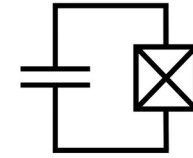
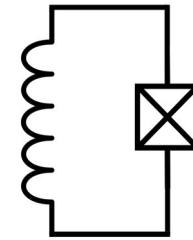
$$E_J \cos(\varphi) + \frac{E_L}{2} \varphi^2$$


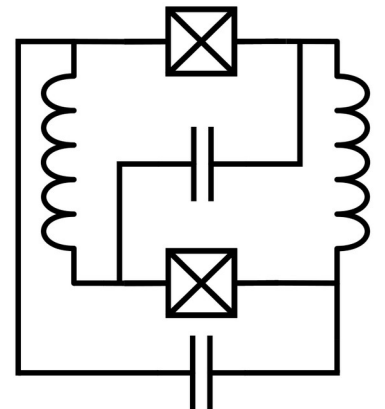
$$- E_J \cos(\varphi_3) - E_J \cos(\varphi_2 - \varphi_1) + \frac{1}{2} E_L (\varphi_2 - \varphi_3)^2 + \frac{1}{2} E_L (\varphi_1)^2$$



Boundary Conditions and Variable Classification

→ Boundary conditions:



- affect the nature of Hilbert space
- influence the choice of basis states

→ How do we get to the boundary conditions? - Potential




→ Degree of Freedom (DoF): periodic and extended

→ 'good' vs 'bad' choice?


$$E_J \cos(\varphi)$$

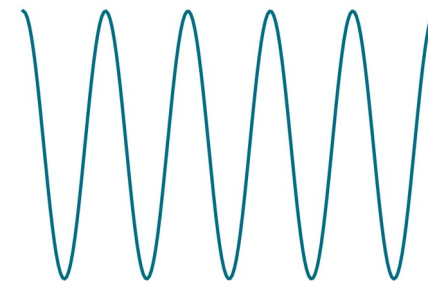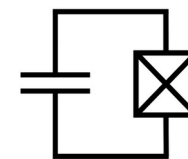
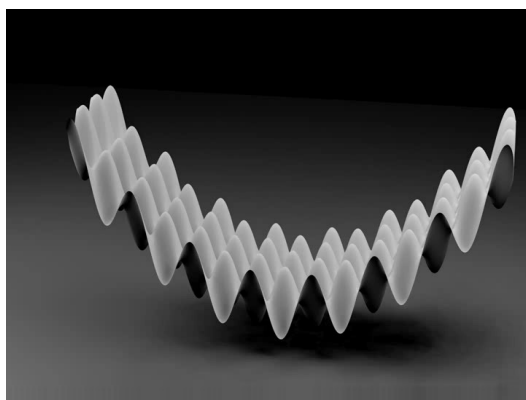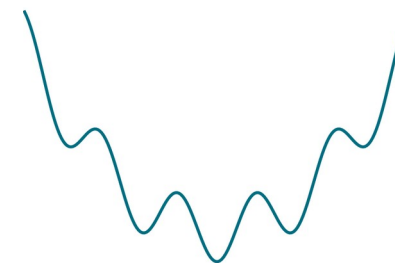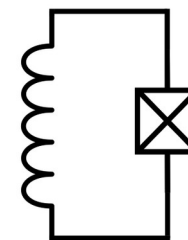
$$E_J \cos(\varphi) + \frac{E_L}{2} \varphi^2$$



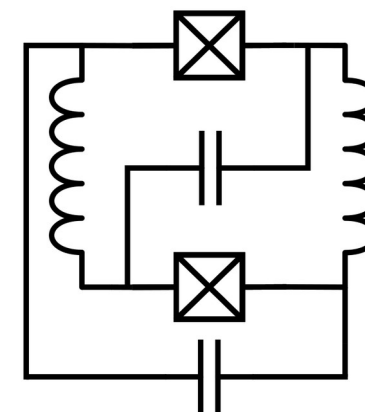
$$- E_J \cos(\varphi_3) - E_J \cos(\varphi_2 - \varphi_1) + \frac{1}{2} E_L (\varphi_2 - \varphi_3)^2 + \frac{1}{2} E_L (\varphi_1)^2$$





Boundary Conditions and Variable Classification


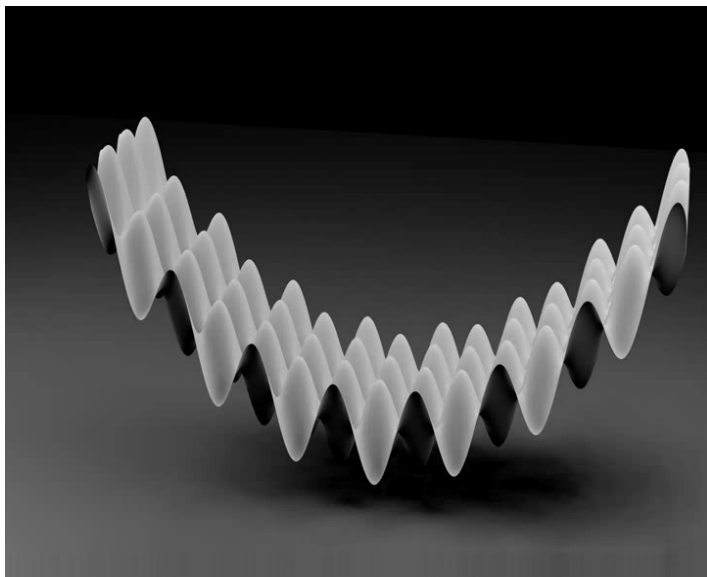
- Boundary conditions:
 - affect the nature of Hilbert space
 - influence the choice of basis states
- How do we get to the boundary conditions? - Potential
- Degree of Freedom (DoF): periodic and extended
- 'good' vs 'bad' choice?
- Special cases: free and frozen



$$E_J \cos(\varphi)$$

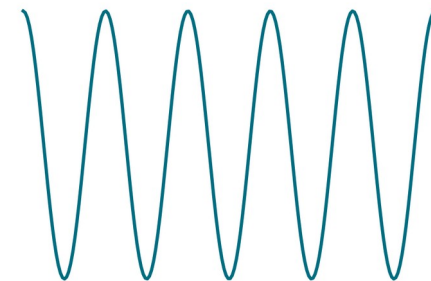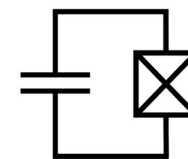
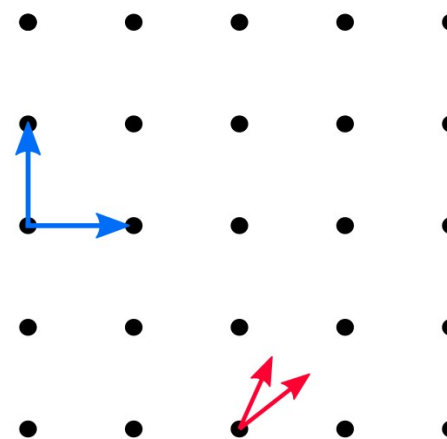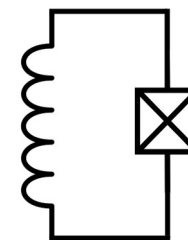
$$E_J \cos(\varphi) + \frac{E_L}{2} \varphi^2$$




Construction of Variables




- How do we identify such variables? - Inspect circuit topology
 - Inductors generate extended DoFs
 - “Islands” generate periodic DoFs
- Eliminate non-dynamical variables
 - Frozen – missing capacitive connections
 - Cyclic – associated with “capacitive islands”

$$\begin{array}{rcl} \varphi_1 & = & \alpha \\ \varphi_2 & = & \frac{1}{2}\beta + \theta \\ \varphi_3 & = & -\frac{1}{2}\beta + \theta \end{array}$$

extended periodic

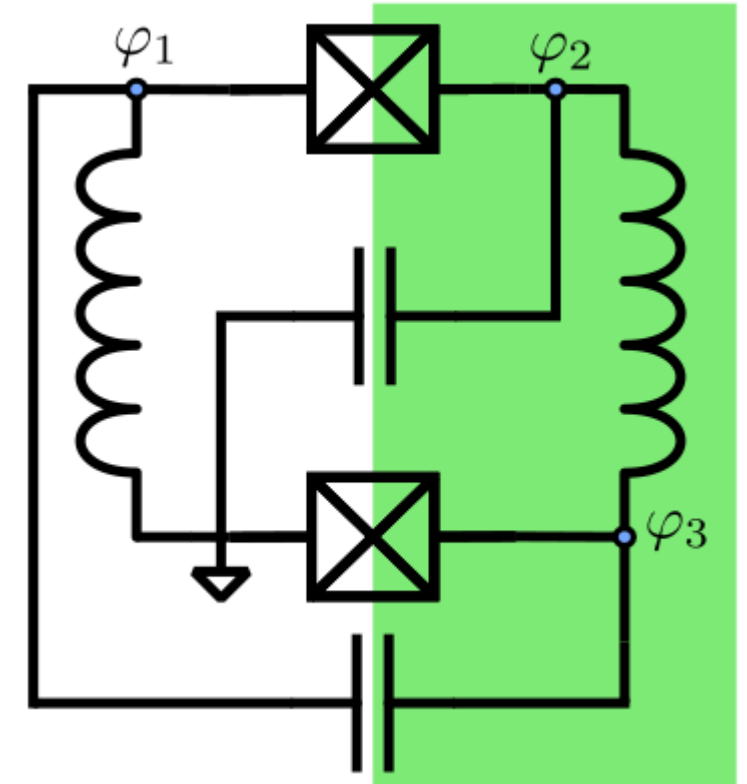


Automating Circuit Quantization

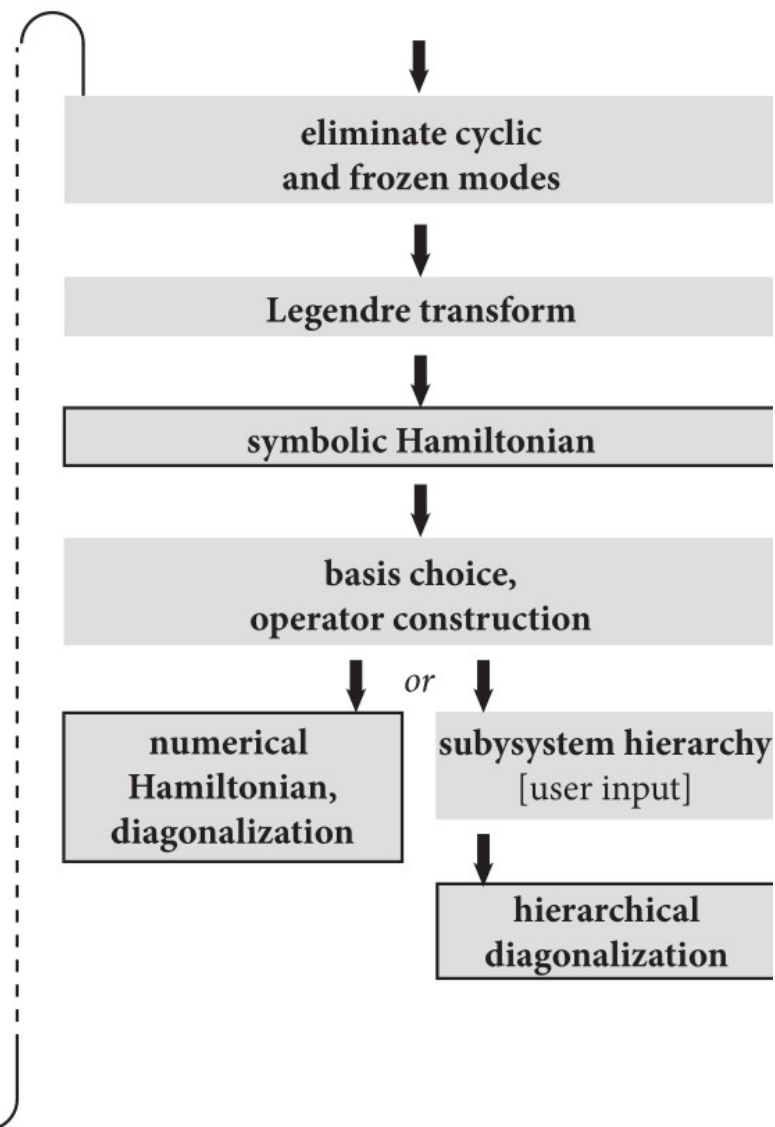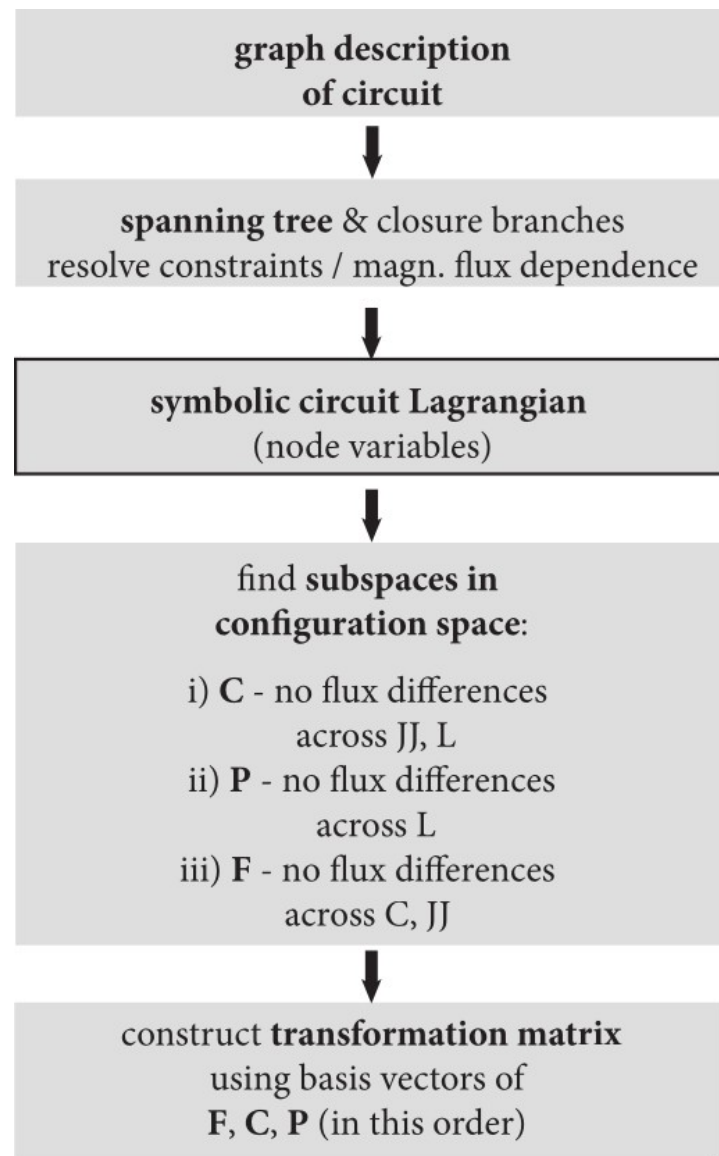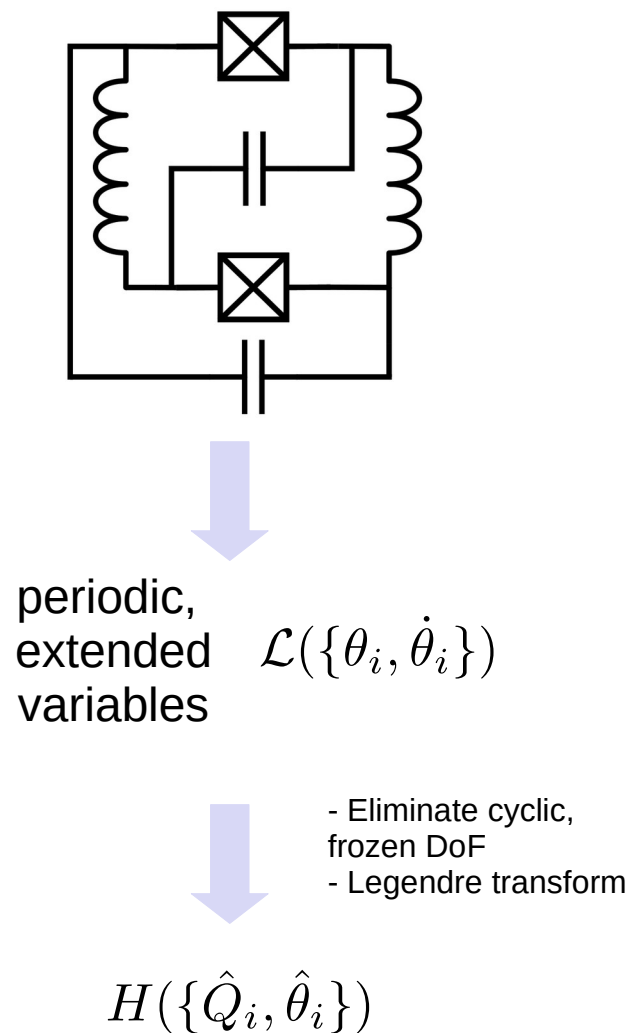

Algorithm and Implementation

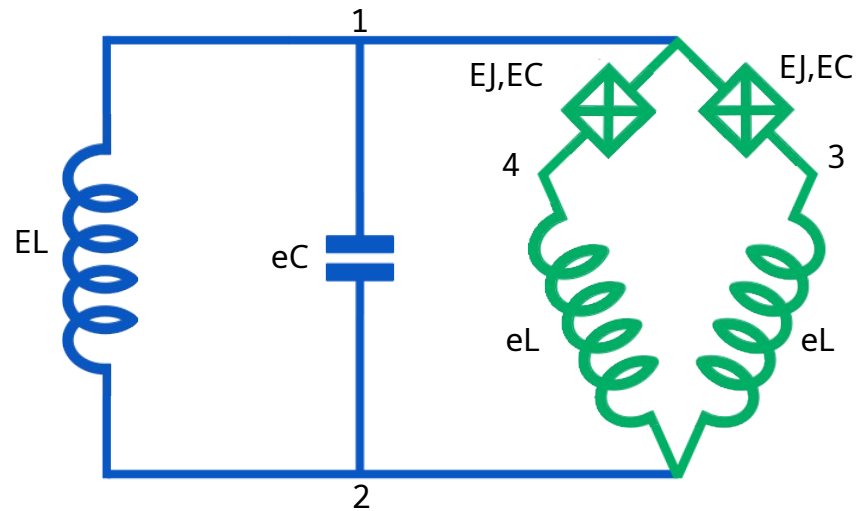
New module to be published in next major release of scqubits



nodes:	4		
branches:			
JJ	1,3	EJ	EC
JJ	1,4	EJ	EC
L	1,2	EL	
C	1,2	eC	
L	2,3	eL	
L	2,4	eL	

Algorithm and Implementation

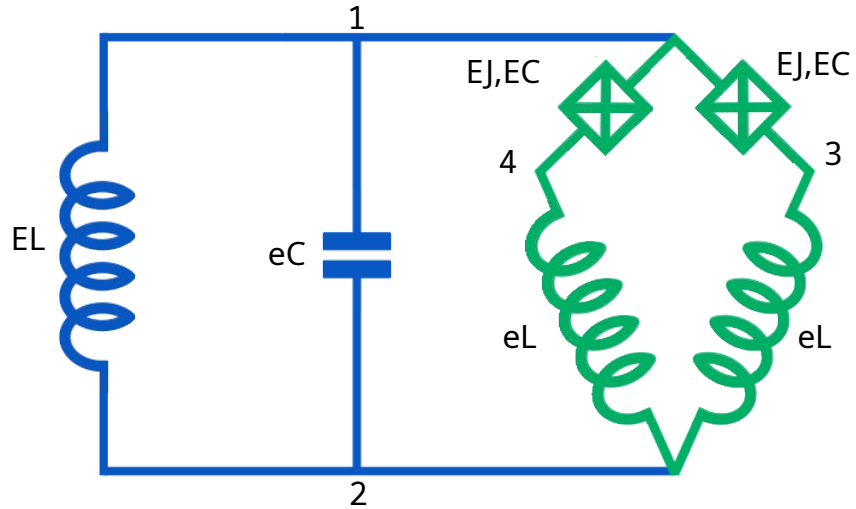New module to be published in next major release of scqubits



nodes: 4
branches:
JJ 1,3 EJ EC
JJ 1,4 EJ EC
L 1,2 EL
C 1,2 eC
L 2,3 eL
L 2,4 eL

```
[1]: import scqubits as scq
```

```
[ ]:
```

